


PROBLEM STATEMENT:

To design and construct a parallel in parallel out and a parallel in serial out shift register

THEORY:


A shift register is a type of sequential logic circuit whose output is primarily determined by its input and previous output. This register contains a collection of Flip Flops that are linked in a cascade fashion, which means that one FF output is simply connected to the input of another FF. This register is used to store and shift a group of binary data. The number of FFs available within the shift register is primarily determined by the number of binary bits stored within the register. For example, if we want to store 4-bit binary data, we need four flip-flops.

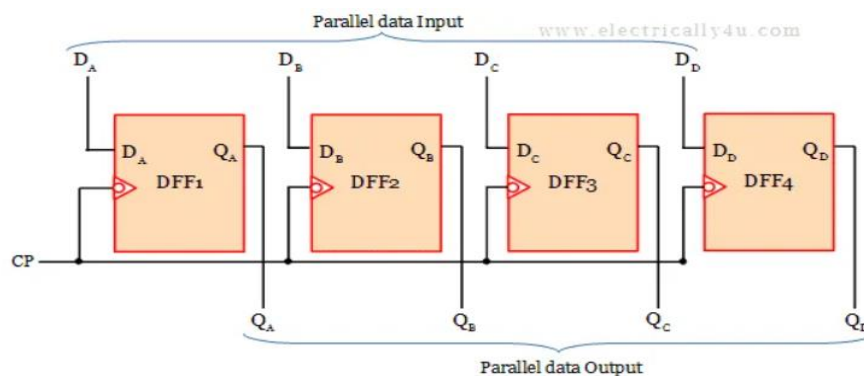Parallel PIPO shift registers are storage devices that perform both data loading and retrieval in parallel. D flip-flops are used to construct the Parallel-in Parallel-out shift register. The four-bit data is received by four flip-flops. When a clock pulse is applied, the loaded data is shifted to the flip-flop's output.



The data is inserted or loaded into each register in parallel in the parallel In Serial Out Shift register, and the inserted data is received serially at the output. Each flip-flop's input is to be loaded with data. At the same time as the clock pulse is applied, the data at each flip-flop's output is moved to the input of the next flip-flop. In order to avoid input conflicts between the loaded and shifted data, the control input is added to this shift register.


If the control input is 0 then AND gates 1, 3, and 5 are disabled and gates 2, 4, and 6 are enabled. It will cause the parallel data at the inputs to be stored in the respective flip-flops. A clock pulse is not needed to load the parallel input data. When the control input is 1, the AND gates 1, 3, and 5 are enabled, while the gates 2, 4, and 6 are disabled. When a clock pulse is applied during this time, the data bit at each flip-flop input is shifted to its output.

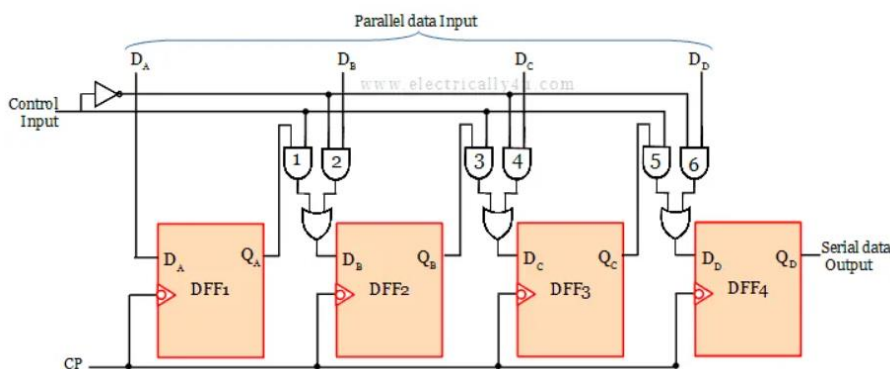

DESIGN:

4bit pipo:

Diagram:

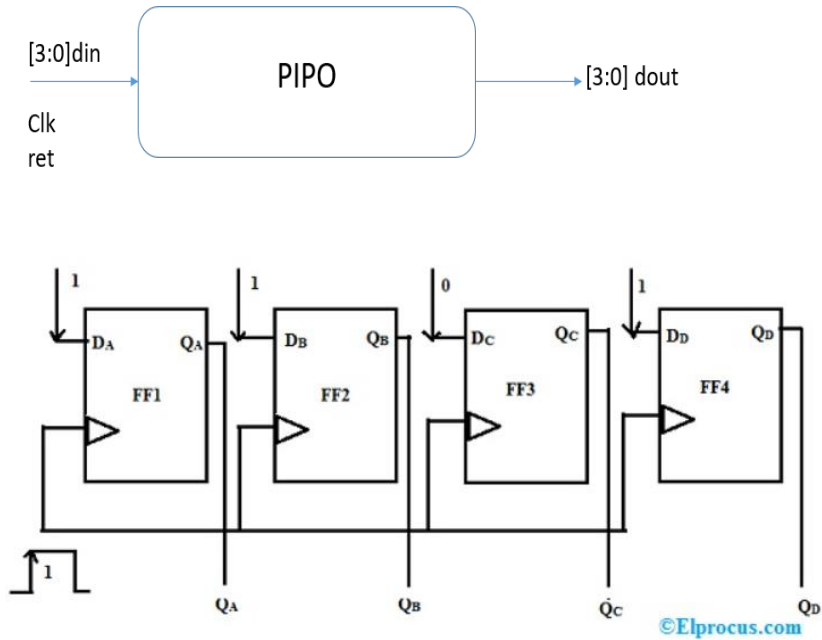


Truth table:



CLK Pulse	QA	QB	QC	QD
0	0	0	0	0
1	1	1	0	1

Timing diagram:

Data shifts on the positive edge clk.

 

4-bit Piso:

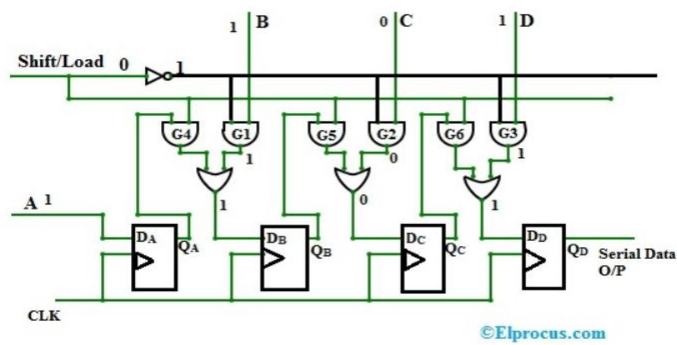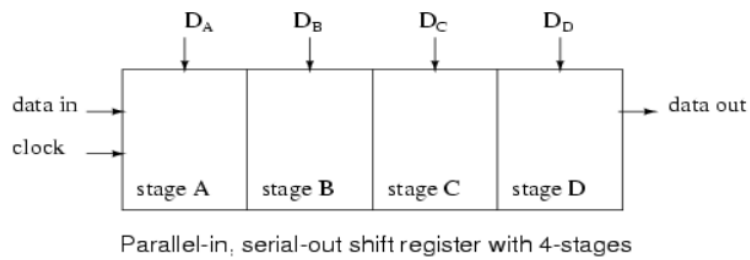

Truth table:


When the signal is load the data is taken as input

D_A	D_B	D_C	D_D
1	1	0	1

When the control signal is shift and clk=1 we get the output.

CLK Pulse	Q_A	Q_B	Q_C	Q_D (Data Output)
0	0	0	0	0
1	1	1	0	1
2	0	1	1	0
3	0	0	1	1
4	0	0	0	1

Timing diagram:

 

HDL CODE:

FOR PIPO:

```
module pipo(
    input logic [3:0] din,
    input logic clk,
    input logic ret,
    output logic [3:0] dout
);
    always_ff @(posedge clk or negedge ret)
    if(!ret) begin
        dout <= 4'b0;
    end
    else
    begin
        dout <= din;
    end
endmodule
```

FOR PISO:

```
module piso(
    input logic clk,
    input logic clr,
    input logic sel,
    input logic [3:0]d,
    output logic sout );
```

```

logic [3:0]q;
always @(posedge clk,posedge clr)
if (clr==1)  q<=4'b0000;
else if(sel==0)  q<=d;
else
begin
sout<=q[0];
q<=q>>1;
end
endmodule

```

COMBINIG BOTH:

```

module parall(
    input logic clk,
    input logic reset,
    input logic load,
    input logic [3:0] din,
    output logic [3:0] dout,
    output logic sout
);
    /* logic clk_div=0;
    logic [27:0]count=0;
    always@ (posedge clk)
    begin
        count<=count+1;
        if(count[27]==1)
        begin
            clk_div<=~(clk_div);
            count<=0;
        end
    end*/
    logic [3:0]temp;
    always_ff @(posedge clk,posedge reset)

```

```

    if(reset) dout<=0;
    else if(load)
        begin
            dout<=din;
            temp<=din;
        end
    else
        begin
            sout<=temp[3];
            temp<={temp[2:0],1'b0};
        end
    endmodule

```

TESTBENCH:

FOR PIPO:

```

For pipo:
module tb();

logic clk,ret;

logic [3:0]din,dout;

pipo dut(din,clk,ret,dout);

initial begin
    ret=1'b0;
    clk=1'b0;
end

initial begin
    forever #40 clk=~clk;
end

initial begin
    din=4'b0010;
    #50 ret=1'b1;
    #25 din=4'b0101;
    #95 din=4'b110;
    #5000 $finish;
end

```

```
endmodule
```

FOR PISO:

```
module tb( );  
    logic clk,clr,sel,sout;  
    logic [3:0] d;  
    piso dut(clk,clr,sel,d,sout);  
    initial begin  
        clk=0;  
        forever #1 clk=~clk;  
    end  
    initial begin  
        clr=1;  
        #2 clr=0;  
        sel=0;  
        d=4'b0100;  
        #4 sel=1;  
        #10 sel=0;  
        d=4'b1110;  
        #2 sel=1;  
        #100 $finish;  
    end  
endmodule
```

COMBINIG BOTH:

```
module tb();  
    logic clk,reset, load,sout;  
    logic [3:0] din,dout;  
    parall dut( clk,reset, load,din,dout,sout);  
    initial begin  
        clk=1'b0;  
    end  
    initial begin  
        forever #40 clk=~clk;
```

```

end

initial begin
reset=1;load=1;din=4'b1000;

#40 reset=0;

#200 load=0;

#200 load=1;


end

endmodule


```

SIMULATION RESULT:


PIPO:

 

PISO:

 


Combining both:


 


SYNTHESISED SCHEMATIC:



For PIPO:

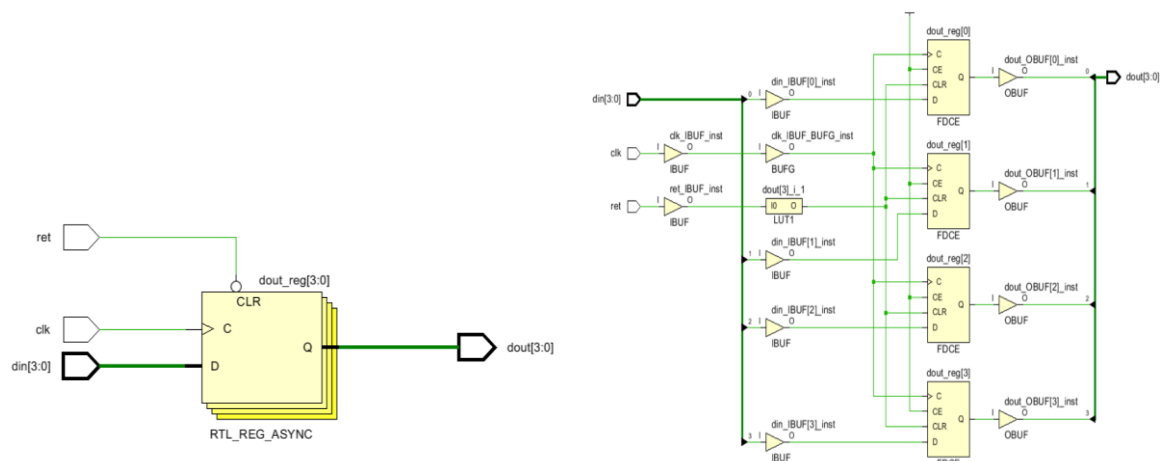

For PISO:

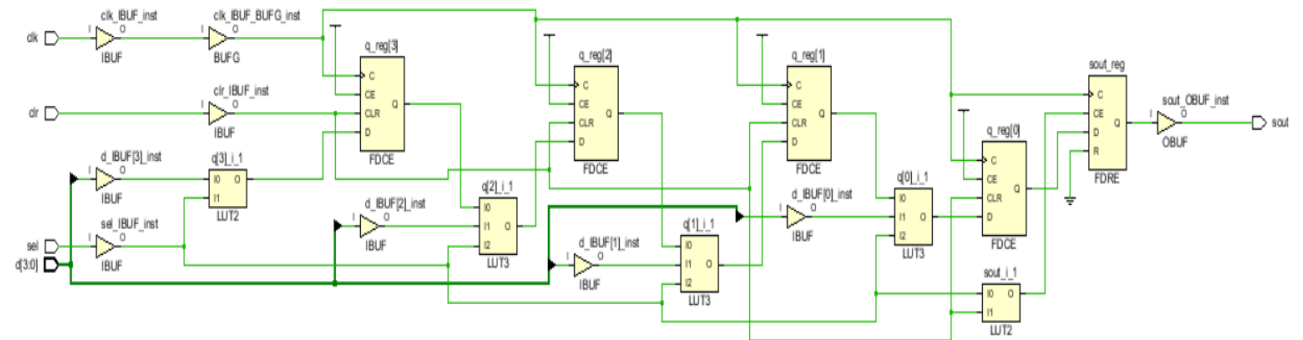 

Combining the circuits:

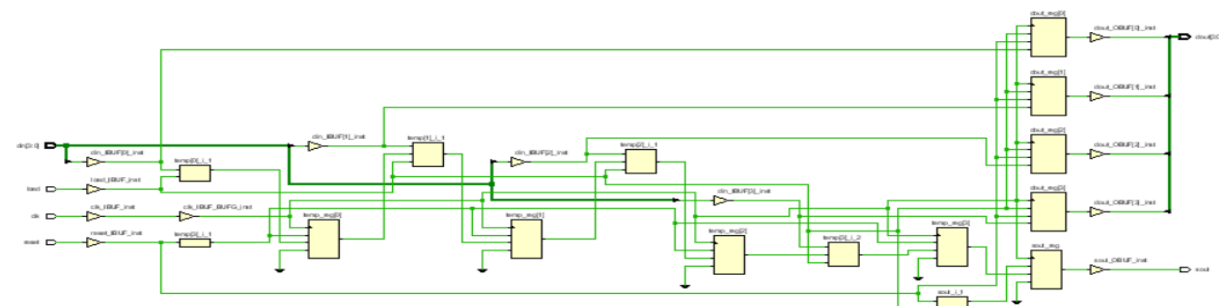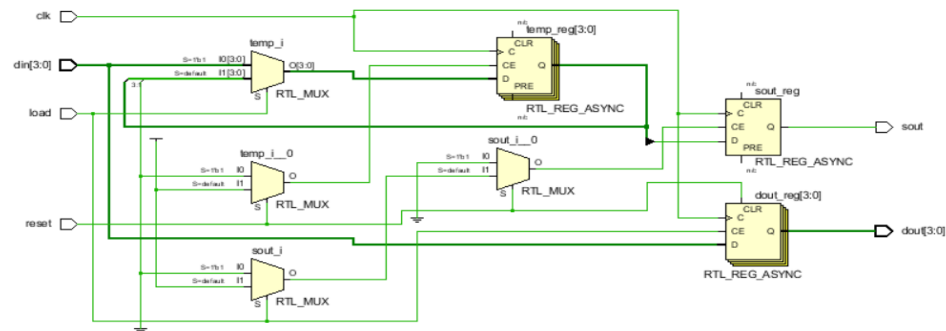

HARDWARE IMPLEMENTATION:


The constrain file is as follows:

All ports (12)												
▼	din (4)	IN			✓	34	LVC MOS33*	▼	3.300			NONE ▼ NONE ▼
	din[3]	IN		R2 ▼	✓	34	LVC MOS33*	▼	3.300			NONE ▼ NONE ▼
	din[2]	IN		T1 ▼	✓	34	LVC MOS33*	▼	3.300			NONE ▼ NONE ▼
	din[1]	IN		U1 ▼	✓	34	LVC MOS33*	▼	3.300			NONE ▼ NONE ▼
	din[0]	IN		W2 ▼	✓	34	LVC MOS33*	▼	3.300			NONE ▼ NONE ▼
▼	dout (4)	OUT			✓	35	LVC MOS33*	▼	3.300	12 ▼	SLOW ▼	NONE ▼ FP_VTT_50 ▼
	dout[3]	OUT		L1 ▼	✓	35	LVC MOS33*	▼	3.300	12 ▼	SLOW ▼	NONE ▼ FP_VTT_50 ▼
	dout[2]	OUT		P1 ▼	✓	35	LVC MOS33*	▼	3.300	12 ▼	SLOW ▼	NONE ▼ FP_VTT_50 ▼
	dout[1]	OUT		N3 ▼	✓	35	LVC MOS33*	▼	3.300	12 ▼	SLOW ▼	NONE ▼ FP_VTT_50 ▼
	dout[0]	OUT		P3 ▼	✓	35	LVC MOS33*	▼	3.300	12 ▼	SLOW ▼	NONE ▼ FP_VTT_50 ▼
Scalar ports (4)												
	clk	IN		W5 ▼	✓	34	LVC MOS33*	▼	3.300			NONE ▼ NONE ▼
	load	IN		T2 ▼	✓	34	LVC MOS33*	▼	3.300			NONE ▼ NONE ▼
	reset	IN		T3 ▼	✓	34	LVC MOS33*	▼	3.300			NONE ▼ NONE ▼
	sout	OUT		U3 ▼	✓	34	LVC MOS33*	▼	3.300	12 ▼	SLOW ▼	NONE ▼ FP_VTT_50 ▼

```
set_property IOSTANDARD LVC MOS33 [get_ports {din[0]}]
set_property IOSTANDARD LVC MOS33 [get_ports {din[1]}]
set_property IOSTANDARD LVC MOS33 [get_ports {din[2]}]
set_property IOSTANDARD LVC MOS33 [get_ports {din[3]}]
set_property IOSTANDARD LVC MOS33 [get_ports {dout[0]}]
set_property IOSTANDARD LVC MOS33 [get_ports {dout[1]}]
set_property IOSTANDARD LVC MOS33 [get_ports {dout[2]}]
set_property IOSTANDARD LVC MOS33 [get_ports {dout[3]}]
set_property PACKAGE_PIN R2 [get_ports {din[3]}]
set_property PACKAGE_PIN T1 [get_ports {din[2]}]
set_property PACKAGE_PIN U1 [get_ports {din[1]}]
set_property PACKAGE_PIN W2 [get_ports {din[0]}]
set_property PACKAGE_PIN L1 [get_ports {dout[3]}]
set_property PACKAGE_PIN P1 [get_ports {dout[2]}]
set_property PACKAGE_PIN N3 [get_ports {dout[1]}]
set_property PACKAGE_PIN P3 [get_ports {dout[0]}]
set_property IOSTANDARD LVC MOS33 [get_ports clk]
set_property PACKAGE_PIN W5 [get_ports clk]
set_property IOSTANDARD LVC MOS33 [get_ports load]
set_property PACKAGE_PIN T2 [get_ports load]
set_property IOSTANDARD LVC MOS33 [get_ports reset]
set_property PACKAGE_PIN T3 [get_ports reset]
set_property PACKAGE_PIN U3 [get_ports sout]
set_property IOSTANDARD LVC MOS33 [get_ports sout]
```

HARDWARE OUTPUT:

 Output obtained for different conditions:



CONCLUSION:

PIPO and PISO circuits find their applications in many digital circuits (for example data storage, manipulation, and transmission). The purpose of the project was to design and build PIPO and PISO, which were served. There is still room for improvement which would take a bit more research.